
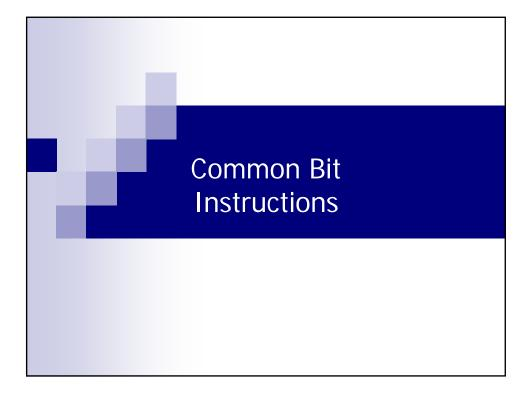


# Topics

- Common Bit Instructions:
  - □ XIC, XIO, OTE, OTL, OTU
- Start/Stop Logic
- One Shot Instructions:
  - □ ONS, OSR, OSF
- Miscellaneous Programming Topics

2

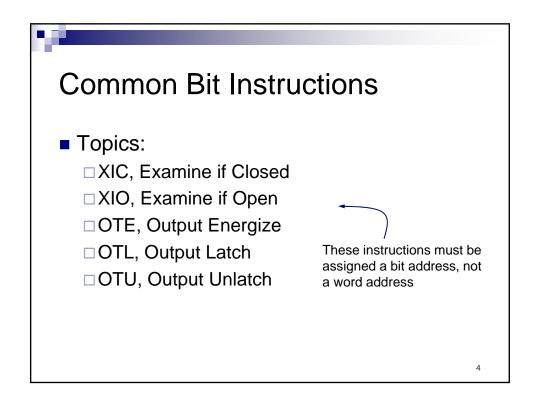






#### Common Bit Instructions

 Bit Instructions are covered in Chapter 1 of the manual entitled "Logix 5000 Controllers – General Instruction Set Reference Manual"

5



# XIC, Examine if Closed

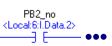

- Also called "Examine On" or "Normally Open input instruction"
- XIC is an input instruction
- The XIC instruction is **true** when the bit it is examining is set to a 1, otherwise it is false.

6

Bit Instructions

3



# XIO, Examine if Open



- Also called "Examine Off" or "Normally Closed input instruction"
- XIO is an input instruction
- The XIO instruction is **true** when the bit it is examining is reset to a **0**, otherwise it is false.

7

### OTE, Output Energize



- Also called a "Coil" instruction
- OTE is an output instruction
- When the rung is true (has logical continuity) the OTE instruction is enabled and will set the bit associated with the OTE instruction. The bit remains set until the rung becomes false.

8

Bit Instructions

Δ



# OTE, Output Energize

- The OTE instruction is non-retentive
- OTE instructions are generally reset (turned off) when:
  - ☐ Switching the processor from the program mode back to the run mode
  - □ Power is restored after a power failure
- The OTE instruction acts like a relay coil

ç



#### OTL, Output Latch




- This is an retentive output instruction
- Retentive → will remain on after a power failure, it must be reset
- When the rung has logical continuity the OTL instruction is enabled and will set the bit associated with the OTL instruction. The bit remains set until it is cleared with an OTU instruction.


10




- This is an output instruction
- The OTU instruction is typically used to clear (reset) a bit which has been latched via an OTL instruction

11

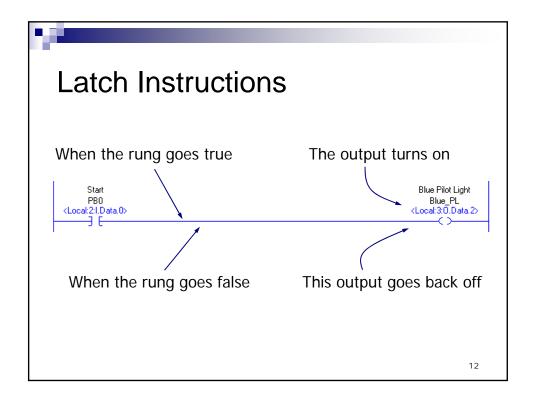

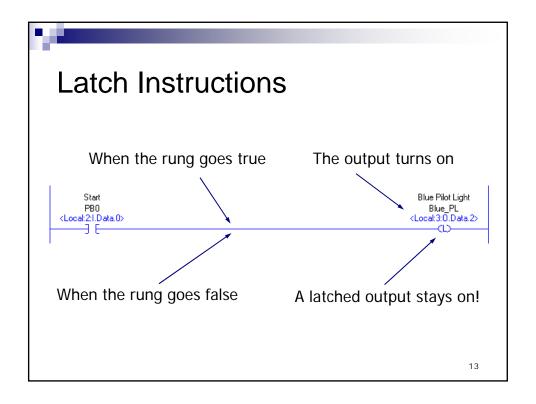

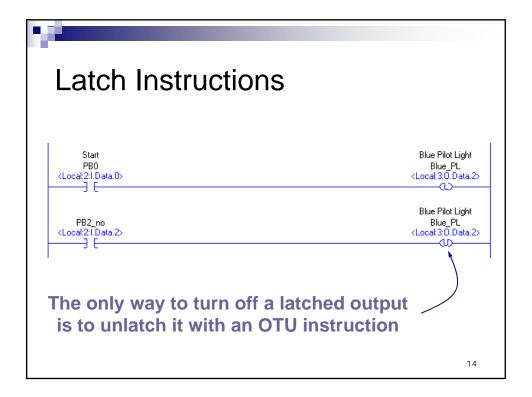








- Latches are retentive:
  - ☐ A latched output will switch ON when the processor is switched back into the RUN mode.
  - ☐ A latched output will switch ON when power is restored after a power failure.


Use latches with caution!


15

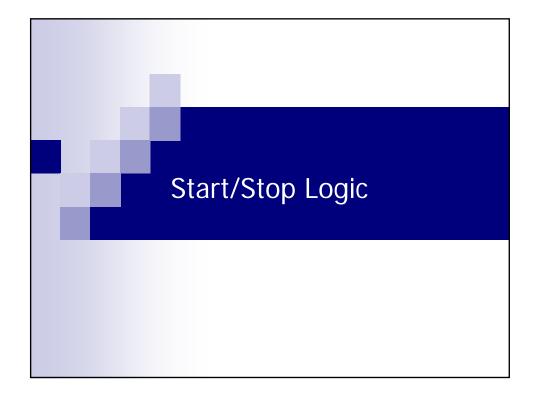


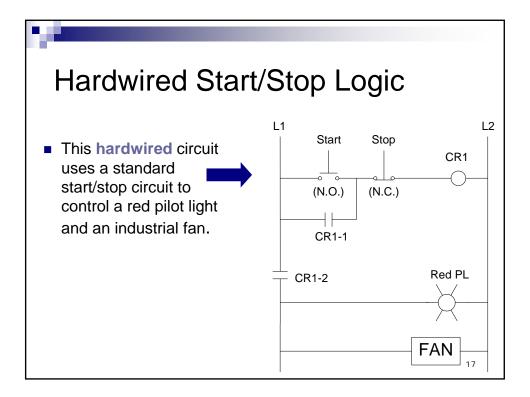


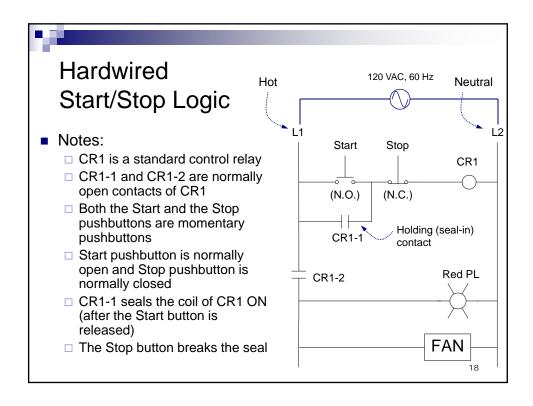


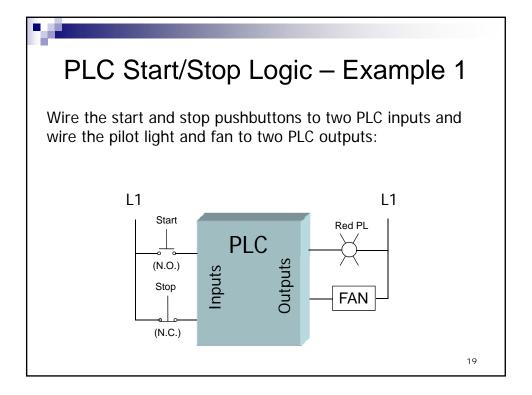


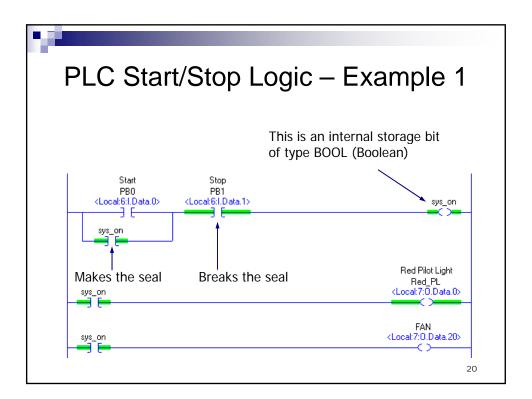


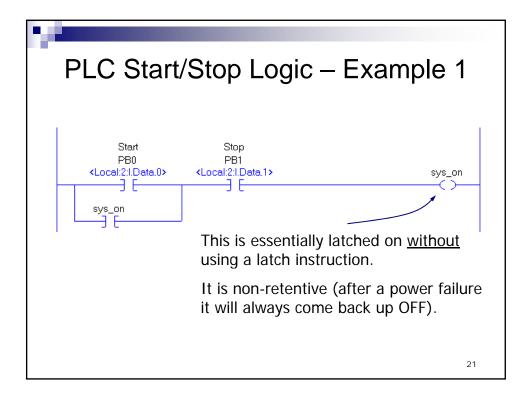


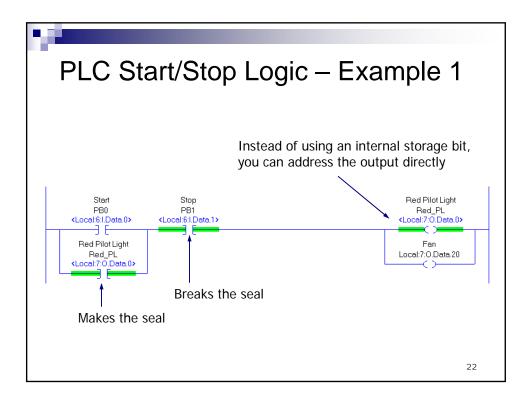


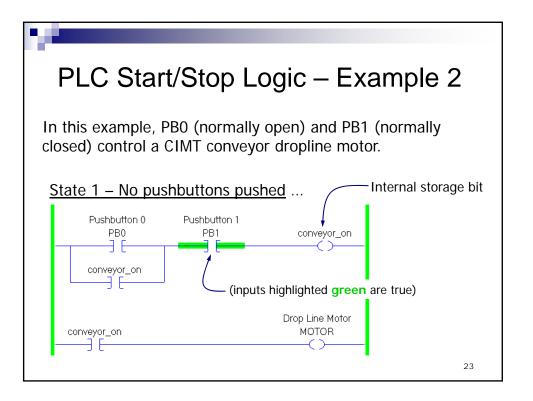


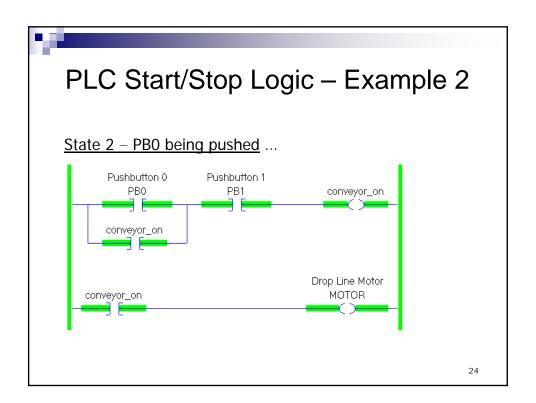


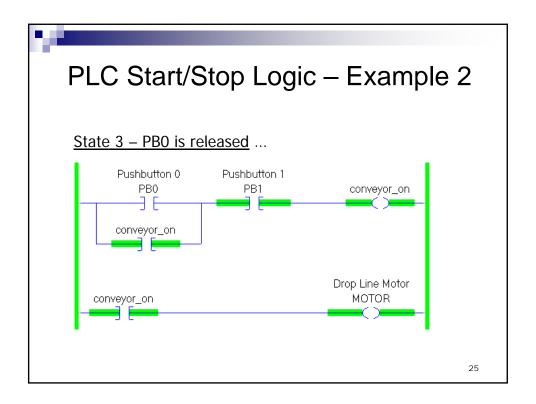


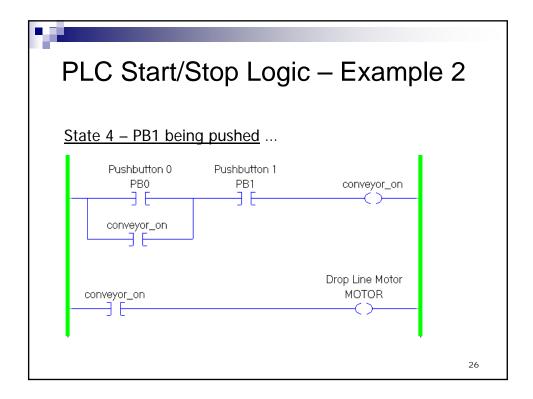


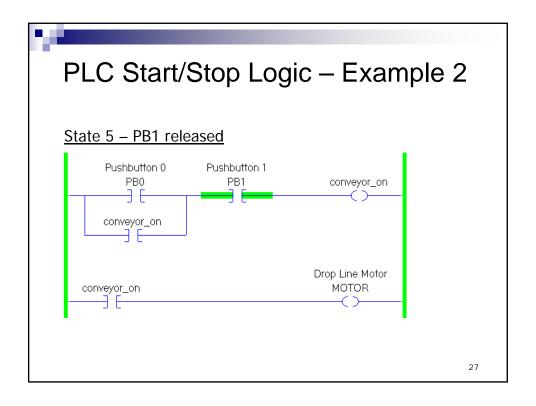

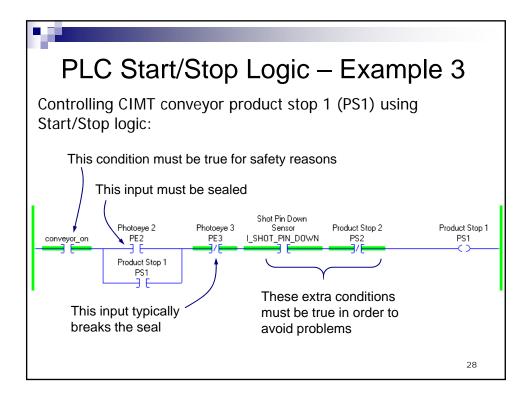

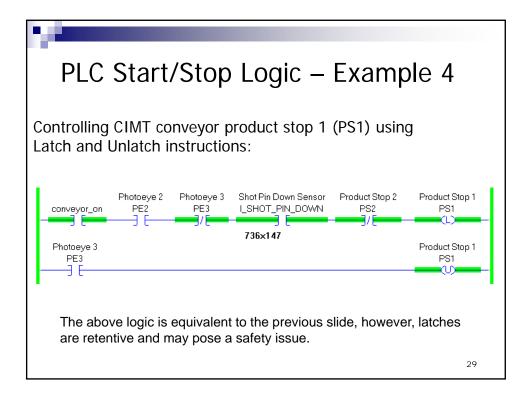

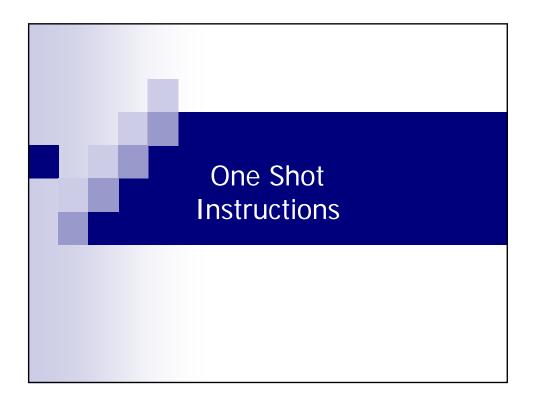

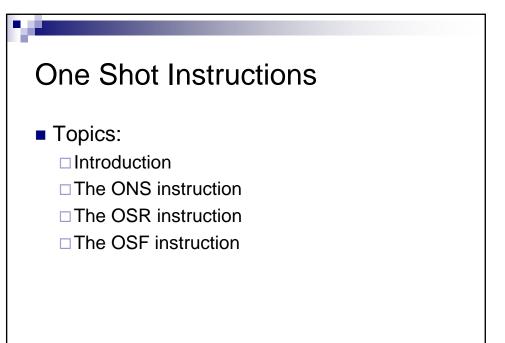

#### Introduction

- One shot instructions are considered bit instructions
- One shots are covered in Chapter 1 of the manual entitled "Logix5000 Controllers – General Instruction Set Reference Manual"

32





#### Introduction


In general, a one shot bit is on for only one program scan


 One shots can be useful when you want something to happen only once per rung transition (false-to-true or true-to-false)


33

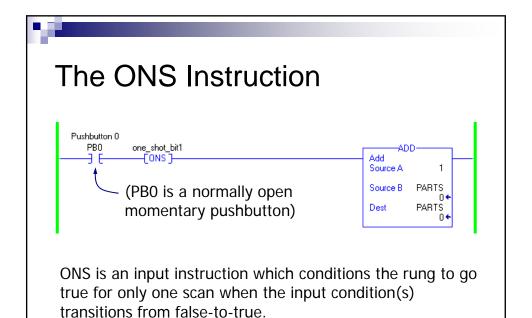


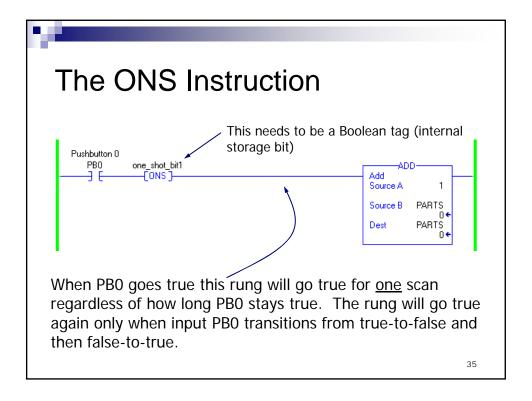


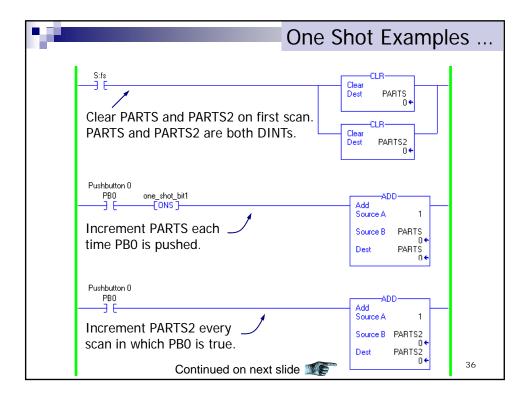


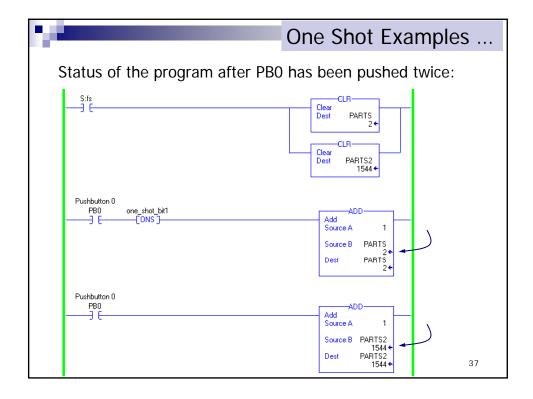


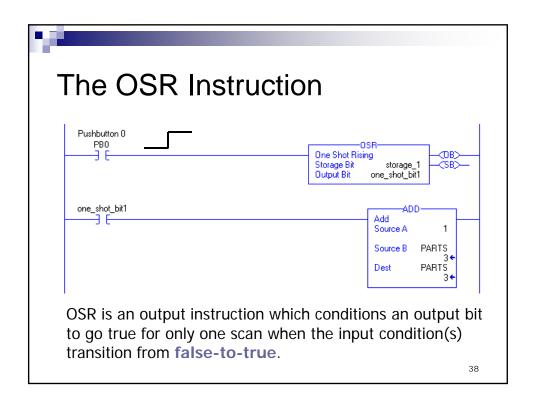


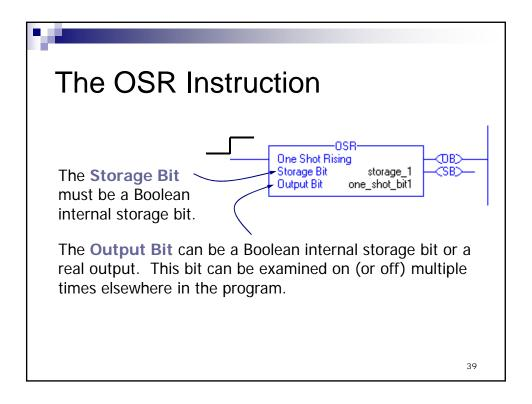


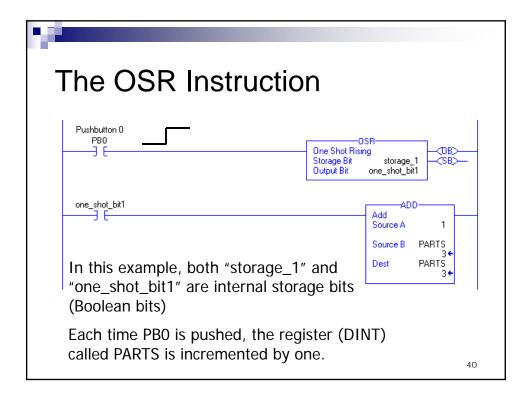

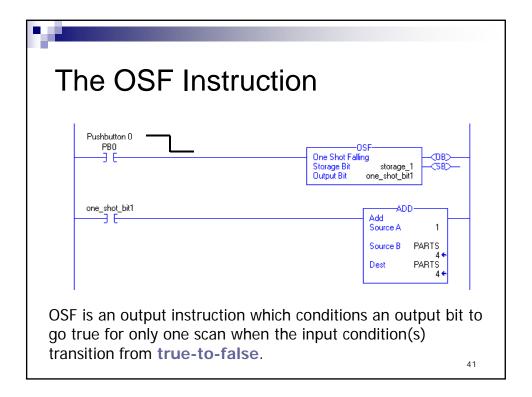

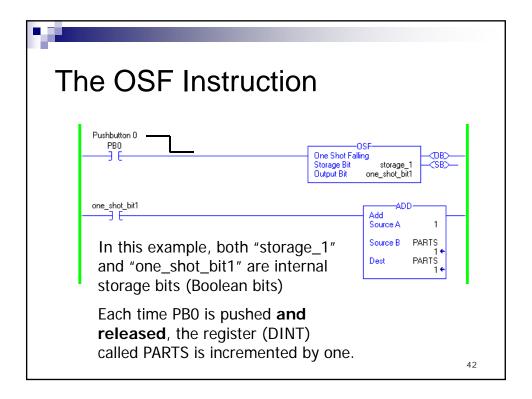

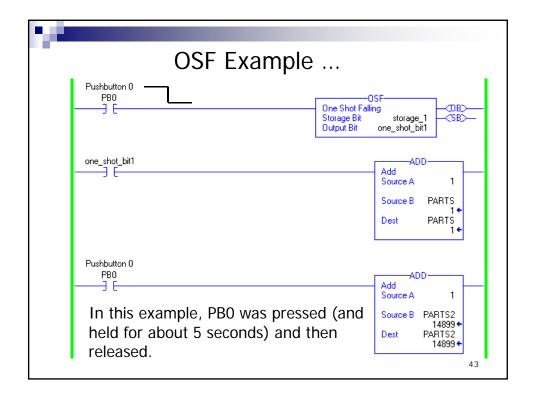

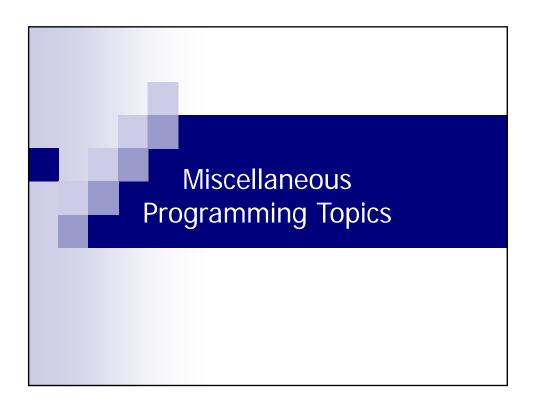






# Multiple Outputs


- ControlLogix programs support multiple output instructions per rung. These output instructions can be:
  - ☐ In parallel on the right side of the rung (parallel branch or nested branch)
  - ☐ In series on the right side of the rung
  - ☐ Between input instructions, as long as the last instruction on the rung is an output instruction


45

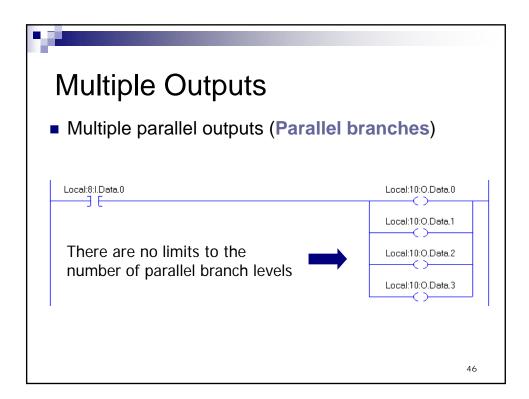


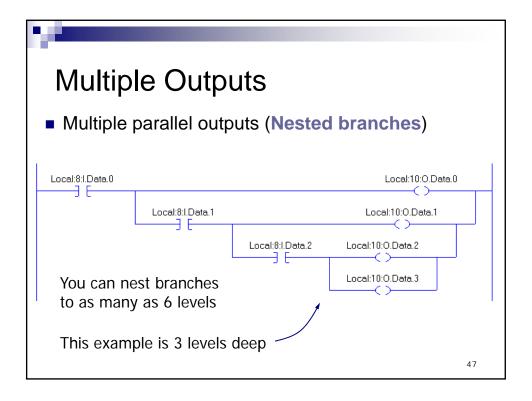


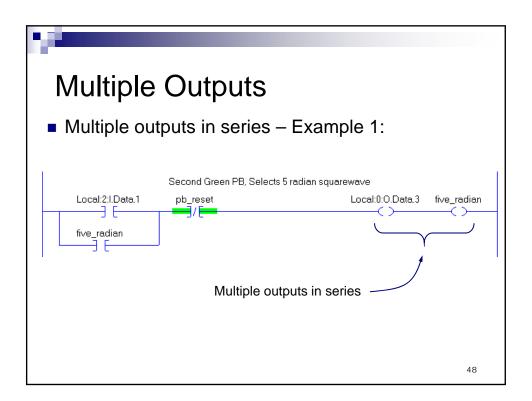

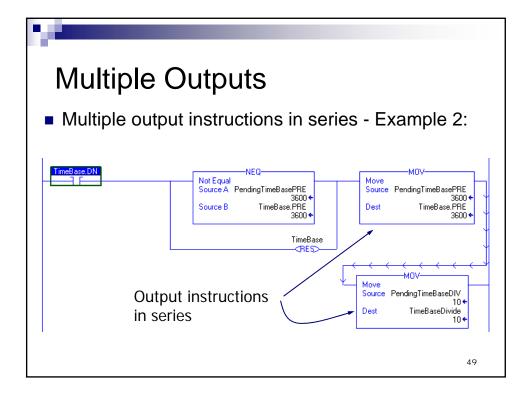

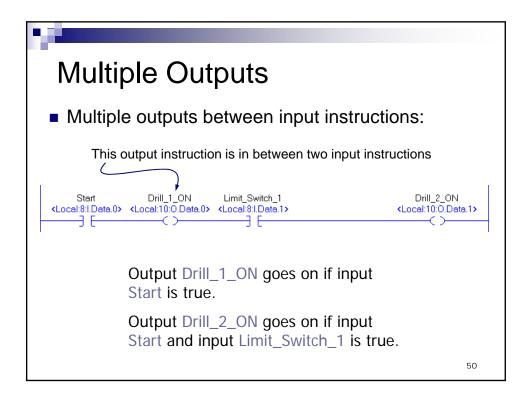

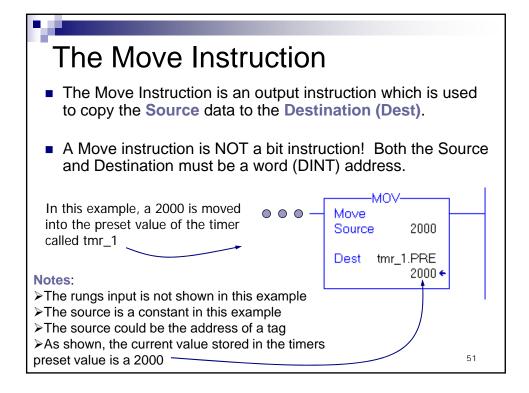

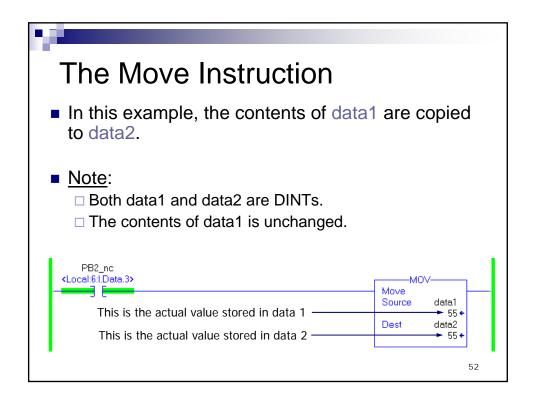



### First Scan Bit, S:FS

- The first scan bit (S:fs) is true for one scan every time the controller is switched from the program mode to the run mode
- Use the first scan bit for initialization purposes
- The first scan bit is a predefined tag
  - ☐ It is not necessary to define a new tag name called "s:fs" (it is predefined for you)

53

